

Electrical Formulas


Review Sheet

Meaning of Variables

| Meaning | Letter | Unit |
|-----------------------|-------------------|-------------------|
| Admittance | $Y = \frac{1}{Z}$ | Siemens (S) |
| Capacitance | C | Farads (F) |
| Capacitive Resistance | X_C | Ohms (Ω) |
| Charge | Q | Coulombs (C) |
| Conductance | $G = \frac{1}{R}$ | Siemens (S) |
| Current | I | Amps (A) |
| Frequency | f | Hertz (Hz) |
| Impedance | Z | Ohms (Ω) |
| Inductive Resistance | X_L | Ohms (Ω) |
| Inductance | L | Henry (H) |
| Reactance | X | Ohms (Ω) |
| Resistance | R | Ohms (Ω) |
| Resistance, Total | R_t | Ohms (Ω) |
| Susceptance | B | Siemens (S) |
| Voltage | E | Volts (V) |

Circuit Diagrams

Series

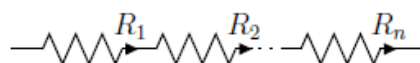

$$R_t = R_1 + R_2 + \dots + R_n$$


Kirchhoff's Circuit Laws

Series


$$V_t = V_1 + V_2 + \dots + V_n$$

$$I_t = I_1 = I_2 = \dots = I_n$$

Parallel

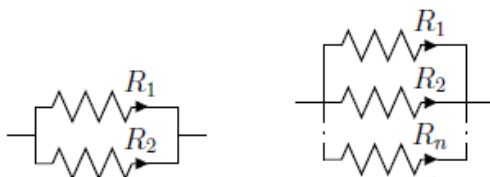
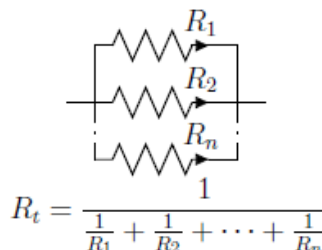
$$R_t = \frac{R_1 \cdot R_2}{R_1 + R_2}$$



$$R_t = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}}$$


Parallel

$$V_t = V_1 = V_2 = \dots = V_n$$

$$I_t = I_1 + I_2 + \dots + I_n$$



Ohm's Law

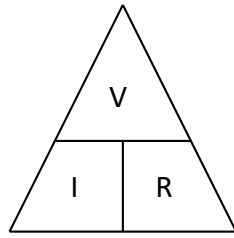

$$V = I R$$

$$R = \frac{V}{I}$$

$$I = \frac{V}{R}$$

Power Formula

$$P = IV = \frac{V^2}{R} = I^2 R = \frac{QV}{t}, \text{ where } t \text{ is time in seconds.}$$

Reactance and Impedance Formulas

| | |
|---------------------------|---------------------------|
| $X = X_L - X_C$ | $Z = R + jX$ |
| $X_C = \frac{1}{2\pi fC}$ | $C = \frac{1}{2\pi fX_C}$ |
| $X_L = 2\pi fL$ | $L = \frac{X_L}{2\pi f}$ |

Resonance Frequency Formula

$$f_r = \frac{1}{2\pi\sqrt{LC}}$$



HUMBER

Content in this document was created by Math & Writing Centre tutors with the support of Student Learning Services and the Faculty of Liberal Arts & Sciences at Humber College.



<https://humber.ca/learningresources/>